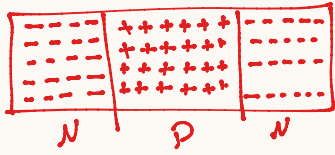


Electronic Switch

↳ it's electronics component → connect & disconnect between two point b/w electricity


example ① transistor ② optocoupler ③ Relay

① transistor → BJT / MOSFET



* NPN


use case
① switching
② Amplification

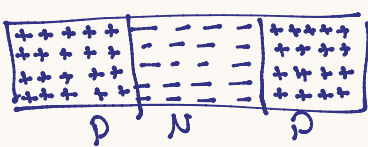

* PNP

* we will use transistor in switching phase?


NPN

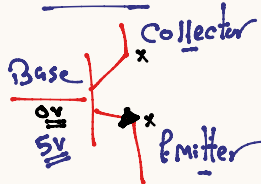

Base = 0
↳ 0.c

Base = 1
↳ 5.c



PNP

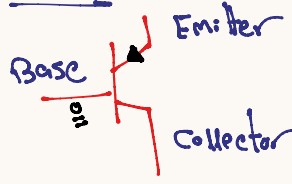


Base = 0 → PNP → 5.c

Base = 1 → PNP → 0.c

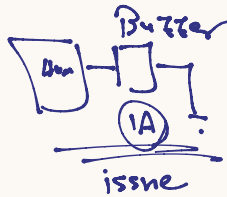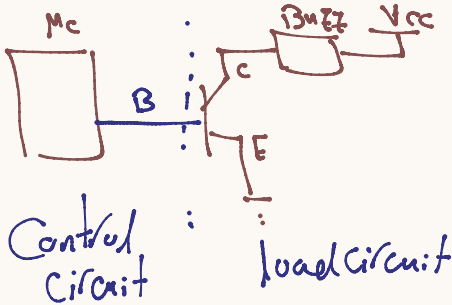* transistor → Isolate between control circuit & load circuit



* optocoupler

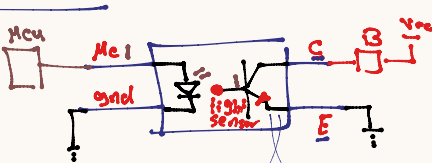

fully isolate between load control.

* 4N35 → PNP
* DC817 → NPN

* How decrease for pin control on motor


* B₁ & B₃ → Mc → A₁
* B₂ & B₄ → Mc → A₂

CW	CCW	off
A ₁ =1	A ₁ =0	A ₁ =0
A ₂ =0	A ₂ =1	A ₂ =0

* Motor


↳ DC Motor →
↳ Stepper →
↳ Servo →

DC Motor → Apply volt → work

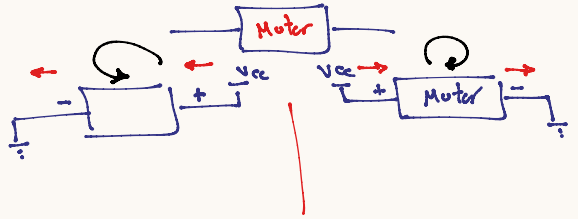

* DC Connection

↳ ① Control on Motor b/w on/off only

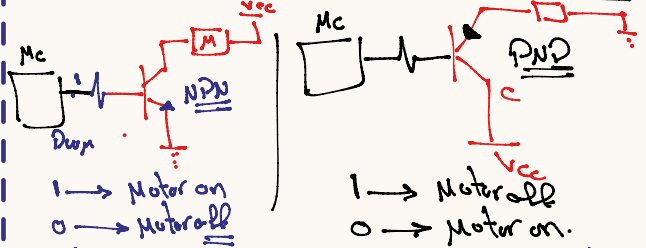

* Note: this connection can be control on motor speed also but must connect with PWM pin

* ② Control DC Motor by Direction


↳ ① off ↳ ② on CW
↳ ③ on CCW

* we need the H-bridge circuit

① transistor

↳ 4NPN ↳ 4PNP ↳ 2NPN / 2PNP

Case → 4NPN

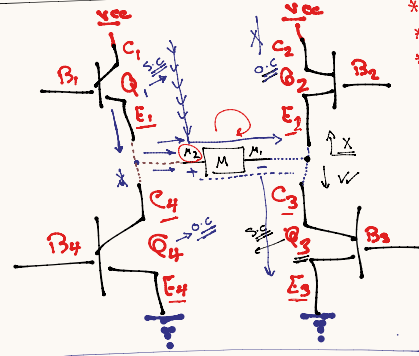


* C₁ & C₂ → 5V
* E₃ & E₄ → Gnd.
* E₁ & C₄ → M₂ (Motor).
* E₂ & C₃ → M₁ (Motor).

B₁ → Mc
B₂ → A₁
B₃ → A₂
B₄ → A₃

Case 1 → CW

Q ₁ → 5.c	B ₁ =1	A ₁ =1
Q ₂ → 0.c	B ₂ =0	A ₂ =0
Q ₃ → 5.c	B ₃ =1	A ₃ =1
Q ₄ → 0.c	B ₄ =0	A ₄ =0

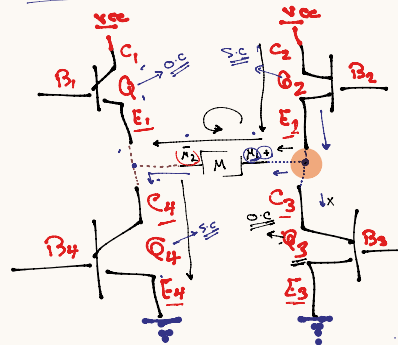


Case 2 → CCW

Q ₁ = 0.c	B ₁ =0	A ₁ =0
Q ₂ = 5.c	B ₂ =1	A ₂ =1
Q ₃ = 0.c	B ₃ =0	A ₃ =0
Q ₄ = 5.c	B ₄ =1	A ₄ =1

Case 3 → off



Q ₁ = 0.c	B ₁ =0	A ₁ =0
Q ₂ = 0.c	B ₂ =0	A ₂ =0
Q ₃ = 0.c	B ₃ =0	A ₃ =0
Q ₄ = 0.c	B ₄ =0	A ₄ =0

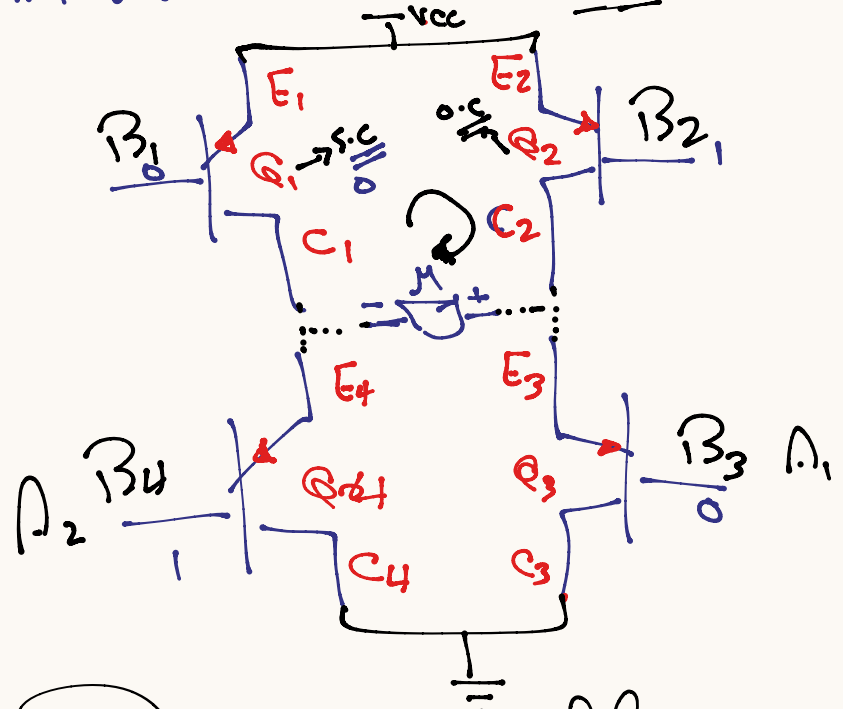* H-bridge $\rightarrow$ 4 transistor PNP



<u>CW</u>	CCW all	
$A_1 = 0$	$A_1 = 1$	$A_1 = 1 (0.c)$
$A_2 = 1$	$A_2 = 0$	$A_2 = 1 (0.c)$

2 NPN - 2 PNP

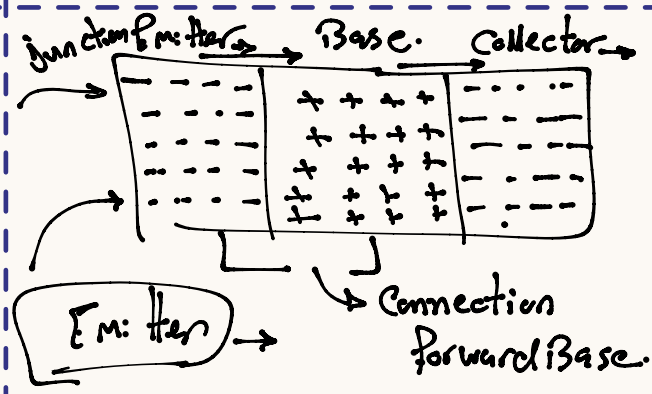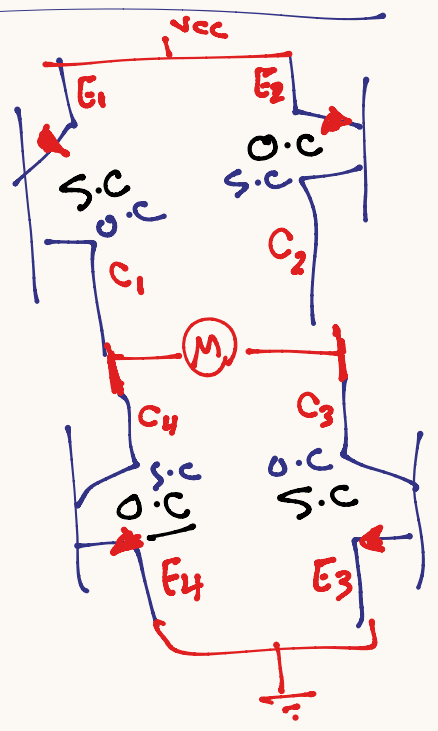

NPN $\rightarrow$ Emitter $\rightarrow$ 0V
 Collector $\rightarrow$ load $\rightarrow$ Vcc

PNP $\rightarrow$ Emitter $\rightarrow$ Vcc
 Collector $\rightarrow$ load $\rightarrow$ 0V

<u>CW</u>	PNP		<u>CCW</u>
$B_1 \rightarrow 0$			$B_1 \Rightarrow 1$
$B_2 \rightarrow 1$			$B_2 \Rightarrow 0$
$B_3 \rightarrow 1$			$B_3 \Rightarrow 0$
$B_4 \rightarrow 0$			$B_4 \Rightarrow 1$
<u>NPN</u>		<u>CW</u>	<u>CCW</u>
$B_1 \rightarrow B_4$	A_1	0	1
$B_2 \rightarrow B_3$	A_2	1	0