

Switches

* its devices connect/disconnect between two point.

* type

① Mechanical Switch

↳ need human power to change between state to another

Push switch

② Electrical Switch

↳ need electricity to change between state to another

transistor
Relay

* Mechanical Connection

- ① External Pullup
 - ② Internal Pullup
 - ③ External Pulldown
- Control bit
1 Pin


iP you need to connect 16 Push Button

↳ 16 Pin from mc



* Key Pad

- ↳ Mechanical switch (Push Button)
- ↳ Connection b/w matrix
- ↳ to minimize no of pin

Key Pad Circuit

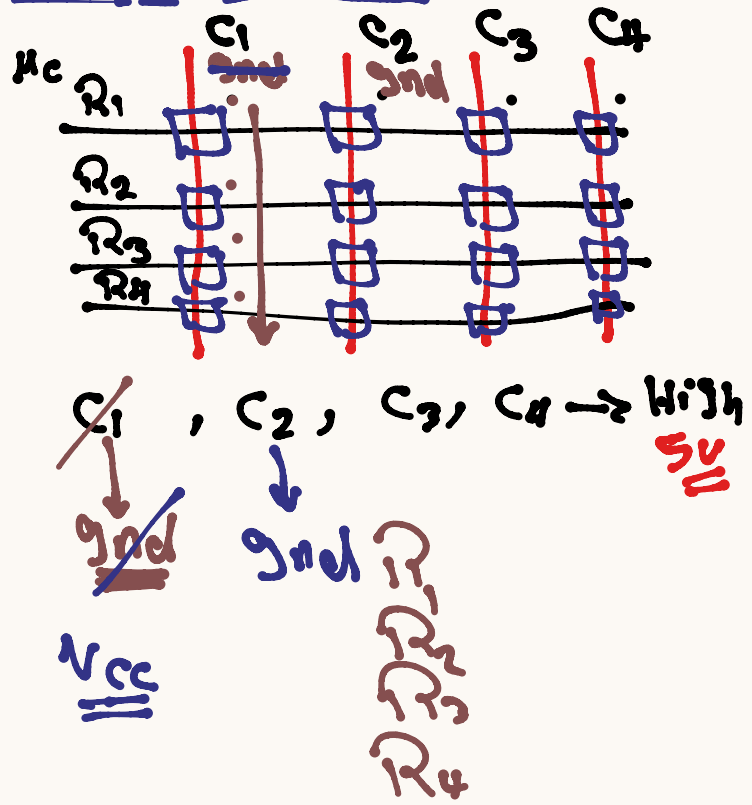

* Normal Button (Internal Pullup)

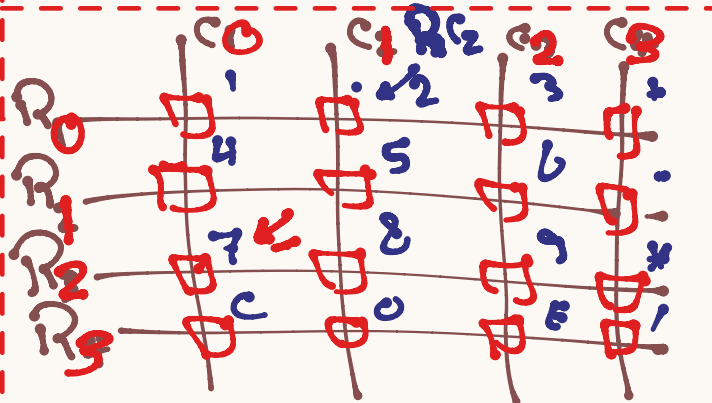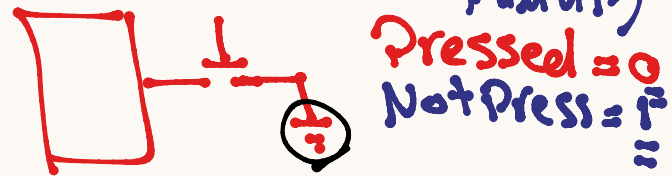

array [R][C]:

{ '1', '2', '3', '+',
'4', '5', '6', '-',
'7', '8', '9', '*',
'C', '0', 'E', '/' }

* $R_0, R_1, R_2, R_3 \rightarrow \underline{\underline{MC}}$
Input
 Internal Pullup.

* $C_0, C_1, C_2, C_3 \rightarrow \underline{\underline{MC}}$
 Output
 Initial High

KPoL Init

* loop (Columns.)
 // Column $\rightarrow$ low End
 loop (Rows)
 Read R
 Return value from array.
 // Column $\rightarrow$ High.

* de bounce

* bus! bus.